

NAME; KAYODE PETER TEMITOPE

MATRIC NUMBER; 208077

DEPARTMENT; COMPUTER SCIENCE (200 Level)

COURSE; DIGITAL LOGIC DESIGNS (CSC 213)

Assignment solution

Let F = Father's input.

A = Abiola's input.

B = Busayo's input.


C = Carol's input.

T = Taiye's input.



K = Kehinde's input.


A logic diagram that will open "door IN"

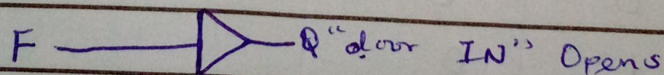Since it's only Mr Felix^{key} that is required before the box opens,



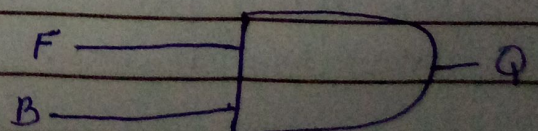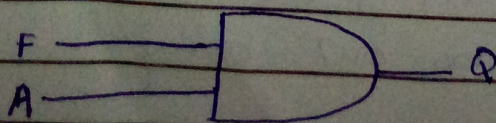
B Logic ~~gate~~^{circuit} diagram that will enable "door OUT" to be opened. For Abiola, Busayo and Carol, their individual keys and the father's key is required to open "door OUT" we have,



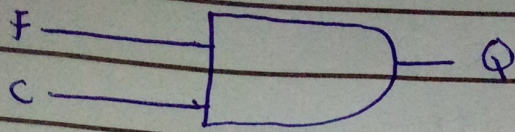


Then, for the twins (Tanya and Kenny), both of them must use their key as well as their father's own for withdrawal.

For Tanya

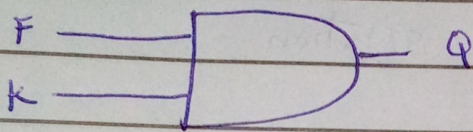

For Kenny:

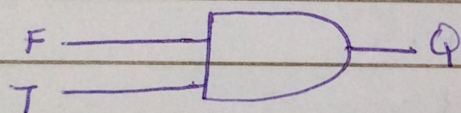

G Truth table for B

X	Y	$X \wedge Y$
0	0	0
0	1	0
1	0	0
1	1	1

The table explains that it's only 1 i.e. True or the door OUT only opens when both inputs are true. i.e. When the father and any of the children uses their key together, the "Door OUT" opens.